

Laboratory 1C: RC and RL circuits

written by: M. Rao

Revision Date: August 30, 2016

Low pass filter using capacitors

Construct the low pass filter as shown in Figure 1. Note that the input voltage applied is 10Vp-p.

Calculate the filter's -3dB frequency point (f_{3dB}). -3dB point is a point where the amplitude drops from by -3dB from the peak. What is the phase shift at different frequencies such as f_{3dB} , $2f_{3dB}$, $4f_{3dB}$, $10f_{3dB}$, and at $0.1f_{3dB}$, $0.01f_{3dB}$.

Draw V_{out}/V_{in} vs Frequency plot in log-log scale in your lab report. Plot also the phase shift with that of Frequency in your lab report.

High pass filter using capacitors

Construct high pass filter as shown in Figure 2. Note that the input voltage applied is 10Vp-p. Calculate the filter's -3dB frequency point (f_{3dB}). Draw V_{out}/V_{in} vs Frequency plot in log-log scale in your lab report. What is the phase shift at different frequencies such as Plot also the phase shift with that of Frequency in your lab report. f_{3dB} , $2f_{3dB}$, $4f_{3dB}$, $10f_{3dB}$, and at $0.1f_{3dB}$, $0.01f_{3dB}$.

RL circuit

Connect the RL circuit as shown in Figure 3. Provide an input voltage of 10Vp-p at a frequency of 700 Hz. Draw V_{out}/V_{in} vs Frequency plot in log-log scale in your lab report for this circuit. Sweep the frequency from 500 Hz to 30 KHz and check f_{3dB} . Change the position of R and L in the circuit and observe the

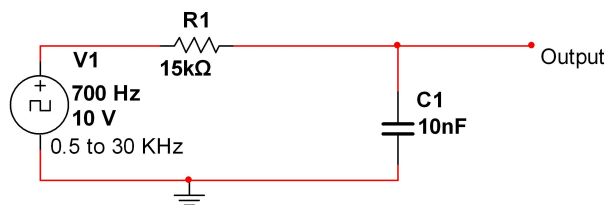


Figure 1: Schematic representation of a Low pass filter circuit using R (15 k Ω) and C components.

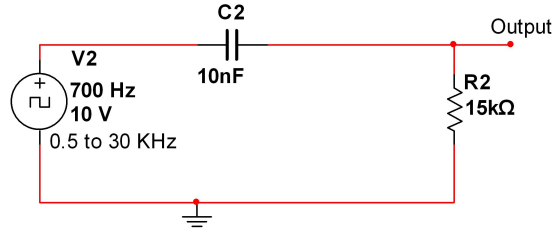


Figure 2: Schematic representation of a High pass filter circuit using R ($5\text{ k } \Omega$) and C components.

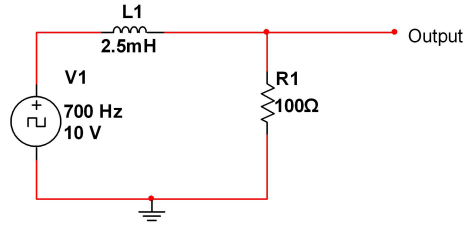


Figure 3: Schematic representation of an RL circuit.

difference in output with respect to previous positions of R and L. What kind of the filter is RL in previous and updated configuration.

RLC circuit

Connect the RLC circuit in series as shown in Figure 4. Provide an input of 2 V_{p-p} . Determine the frequency where the output is very high. This frequency is called resonance frequency of this circuit. Plot the frequency response for this circuit. Remember frequency response suggests Output voltage versus frequency. Now apply a square wave of 2 V_{p-p} at the resonance frequency and check the output. Slowly decrease the frequency and observe decrease in output voltage. Decrease the frequency till you observe a sudden rise in the output voltage. Again note down the output voltage and input frequency. Repeat this till you find one more rise in the output voltage. Draw a table consisting of three output voltage and three input frequency. Do you see any relation between amplitudes and frequencies? The peak frequency reduced by $1/3^{\text{rd}}$, the amplitude reduces close to $1/3^{\text{rd}}$ and similarly the frequency reduced by $1/5^{\text{th}}$, the amplitude reduces by $1/5^{\text{th}}$. (The circuit works as a fourier analyzer detecting ($1/3^{\text{rd}}$ term) and ($1/5^{\text{th}}$ term)). You may not appreciate the circuit at this level, but bring it back when you learn Signals and Systems course. This is one of the circuit which had revolutionized signal processing in hardware.

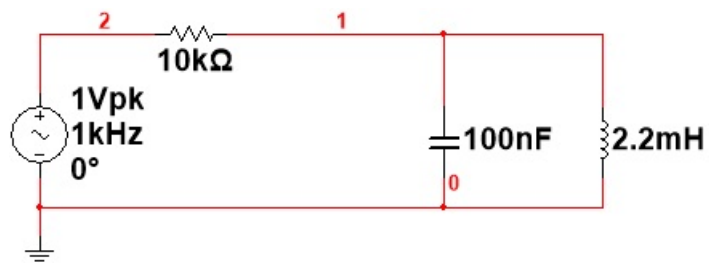


Figure 4: Schematic representation of an RLC circuit.